

**Practical Manual
Lab: DSD
(EE-330)**

Electronics and Communication Engg. (ECE/CSE)



***RAO PAHALD SINGH GROUP OF INSTITUTIONS
BALANA(MOHINDER GARGH)123029***

EXPERIMENT 1

Aim:-

Write the vhdl code and simulate it for the following gates.

- i) Two i/p AND Gates.
- ii) Two i/p OR Gates.
- iii) Two i/p NAND Gates
- iv) Two i/p NOR Gates.
- v) Two i/p EX-OR Gates.
- vi) NOT Gates.

SPECIFICATION OF APPARATUS USED:-

Mentor graphics FPGA advantage software modelsim simulation tool.

Program:-


- i) **Behavior Model if two i/p AND Gate.**

```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_arith.all;
```

```
Entity and2 is
Port (a, b: in bit; z: out bit);
End and2;
```

```
Architecture beh of and2 is
Begin process (a, b)
Begin
If (a='0' and b='0') then
Z<='0';
ElsIf (a='0' and b='1') then
Z<='0';
ElsIf (a='1' and b='0') then
Z<='0';
ElsIf (a='1' and b='1') then
Z<='1';
End if;
End process;
End beh;
```

EXPERIMENTAL SET UP:-

 

TRUTH TABLE

a	b	z
0	0	0
0	1	0
1	0	0
1	1	1

Logic Equation: $Z = a \text{ AND } b$


ii) Behavior Model if two i/p OR Gates

```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_arith.all;
```

```
Entity OR_2 is
Port (a, b: in bit; z: out bit);
End OR_2;
```

```
Architecture OR_2_beh of OR_2 is
Begin process (a,b)
Begin
If (a='0' and b='0') then
Z<='0';
Elsif (a='0' and b='1') then
Z<='1';
Elsif (a='1' and b='0') then
Z<='1';
Elsif (a='1' and b='1') then
Z<='1';
End if;
End process;
End OR_2_beh;
```

EXPERIMENTAL SET UP:-

 

TRUTH TABLE

a	b	Z
0	0	0
0	1	1
1	0	1
1	1	1

Logic Equation: $Z = a \text{ OR } b$


iii) Behavior Model if two i/p NAND Gate

```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_arith.all;
```

```
Entity NAND_2 is
Port (a, b: in bit; z: out bit);
End NAND_2;
```

```
Architecture NAND_2_beh of NAND_2 is
Begin process (a, b)
Begin
If (a='0' and b='0') then
Z<='1';
Elsif (a='0' and b='1') then
Z<='1';
Elsif (a='1' and b='0') then
Z<='1';
Elsif (a='1' and b='1') then
Z<='0';
End if;
End process;
End NAND_2_beh;
```

EXPERIMENTAL SET UP:-

 

NAND_2 TRUTH TABLE

a	b	Z
0	0	1
0	1	1
1	0	1
1	1	0

Logic Equation: $Z = a \text{ AND } b$


iv) Behavior Model if two i/p NOR Gates

Library IEEE;
 Use IEEE.std_logic_1164.all;
 Use IEEE.std_logic_arith.all;

Entity NOR_2 is
 Port (a, b: in bit; z: out bit);
 End NOR_2;

Architecture NOR_2_beh of NOR_2 is
 Begin process (a, b)
 Begin
 If (a='0' and b='0') then
 Z<='1';
 Elsif (a='0' and b='1') then
 Z<='0';
 Elsif (a='1' and b='0') then
 Z<='0';
 Elsif (a='1' and b='1') then
 Z<='0';
 End if;
 End process;
 End NOR_2_beh;

EXPERIMENTAL SET UP:-

 

NOR_2

TRUTH TABLE

a	b	Z
0	0	1
0	1	0
1	0	0
1	1	0

Logic Equation: $Z = a \text{ OR } b$


(iv) Behavior Model if two i/p EX-OR Gates

```
Library IEEE;
Use IEEE.std_logic_1164_all;
Use IEEE.std_logic_arith_all;
```

```
Entity EXOR_2 is
Port (a, b: in bit; z: out bit);
End EXOR_2;
```

```
Architecture EXOR_2_beh of EXOR_2 is
Begin
Process (a, b)
Begin
If (a='0' and b='0') then
Z<='0';
Elsif (a='0' and b='1') then
Z<='1';
Elsif (a='1' and b='0') then
Z<='1';
Elsif (a='1' and b='1') then
Z<='0';
End if;
End process;
End EXOR_2_beh;
```

EXPERIMENTAL SET UP:-

 

EX-OR_2

TRUTH TABLE

a	b	Z
0	0	0
0	1	1
1	0	1
1	1	0

Logic Equation: $Z = a \text{ EX-OR } b$


v) Behavior Model of NOT Gate

```
Library IEEE;
Use IEEE.std_logic_1164_all;
Use IEEE.std_logic_arith_all;
```

```
Entity NOT_2 is
Port (a: in bit; z: out bit);
End NOT_2;
```

```
Architecture EXOR_2_beh of EXOR_2 is
Begin
Process (a)
Begin
If (a='0') then
Z<='1';
Elsif (a='1') then
Z<='0';
End if;
End process;
End NOT_2_beh;
```

EXPERIMENTAL SET UP:-

 

Precautions:-

Make sure that there is no syntax and semantic error.

Result:-

All the VHDL codes of AND, OR, NAND, NOR, EX-OR and NOT gates are simulated and find correct

EXPERIMENT 2

Aim:-

Write the VHDL code and simulate it for Comparator.

SPECIFICATION OF APPARATUS USED:-

Mentor Graphics FPGA Advantage Software Modelsim Simulation Tool.

Program:-


```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_arith.all;
```

```
Entity CMP_2 is
Port (a, b: in bit; ALB, AGB, AEB: out bit);
End CMP_2;
```

Architecture CMP_2_beh of CMP_2 is

```
Begin
Process (a, b)
Begin
If (a='0' and b='0') then
ALB<='0';
AGB<='0';
AFB<='1';
Elsif (a='0' and b='1') then
ALB<='1';
AGB<='0';
AFB<='0';
Elsif (a='1' and b='0') then
ALB<='0';
AGB<='1';
AFB<='0';
Elsif (a='1' and b='1') then
ALB<='0';
AGB<='0';
AFB<='1';
End if;
End process;
End CMP_2_beh;
```

EXPERIMENTAL SET UP:-

 

Precautions:-

Make sure that there is no syntax and semantic error.

Result:-

All the VHDL codes of 1- bit Comparator is simulated and synthesized.

EXPERIMENT NO.-3

Aim:-

Write a program for behavior model of 4- bit Comparator

SPECIFICATION OF APPARATUS USED:-

Mentor Graphics FPGA Advantage Software Modelsim Simulation Tool.

Program:-

```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_arith.all;
```

```
Entity COM_2 is
Port (a, b: in bit_Vector (3 down to 0); z: out bit_vector (2 down to 0));
End COM_2;
```

```
Architecture COM_2_beh of COM_2 is
Begin
Process (a, b)
Begin
If (a=b) then
Z<='100';
Elsif (a<b) then
Z<='010';
Elsif (a>b) then
Z<='001';
End if;
End process;
End COM_2_beh;
```

Precautions:-

Make sure that there is no syntax and semantic error.

Result:-

All the VHDL codes of 4- bit Comparator is simulated and synthesized.

EXPERIMENT NO.-4

Aim:-

Write the VHDL code and simulate it for 4:1 mux and 4:1 demultiplexer.

SPECIFICATION OF APPARATUS USED:-

Mentor graphics FPGA advantage software modelsim simulation tool.


Program: - Multiplexer's Behavior Model

```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_arith.all;
```

```
Entity MUX_2 is
Port (i0, i1, i2, i3, s0, s1: in bit; z: out bit);
End MUX_2;
```

```
Architecture MUX_2_beh of MUX_2 is
Begin
Process (so, s1)
Begin
If (s1='0' and s0='0') then
Z<='i0';
Elsif (s1='0' and s0='1') then
Z<='i1';
Elsif (s1='1' and s0='0') then
Z<='i2';
Elsif (s1='1' and s0='1') then
Z<='i3';
End if;
End process;
End MUX_2_beh;
```

EXPERIMENTAL SET UP:-

 

Select Input's S1 S0	Output Y
0 0	I0
0 1	I1
1 0	I2
1 1	I3

Truth table of 4-to-1 Multiplexer

Program: - Behavior Model of Demultiplexer (1 to 4)

```
Library IEEE;
Use IEEE.std_logic_1164_all;
Use IEEE.std_logic_arith_all;
```

```
Entity DEMUX_2 is
Port (a, s0, s1: in bit; z: out bit_vector (3 down to 0));
End DEMUX_2;
```

```
Architecture DEMUX_2_beh of DEMUX_2 is
```

```
Begin
Process (so, s1)
Begin
If (s1='0' and s0='0') then
```

```

Z (0) <=a;
Z (1) <='0';
Z (2) <='0';
Z (3) <='0';
Elsif (s1='0' and s0='1') then
Z (0) <='0';
Z (1) <=a;
Z (2) <='0';
Z (3) <='0';
Elsif (s1='1' and s0='0') then
Z (0) <='0';
Z (1) <='0';
Z (2) <=a;
Z (3) <='0';
Elsif (s1='1' and s0='1') then
Z (0) <='0';
Z (1) <='0';
Z (2) <='0';
Z (3) <=a;
End if;
End process;
End DEMUX_2_beh;

```

Precautions:-

Make sure that there is no syntax and semantic error.

Result:-

- A) All the VHDL codes of 4 to 1 Multiplexer is simulated and synthesized.
- B) All the VHDL codes of 4 to 1 Demultiplexer is simulated and synthesized.

EXPERIMENT NO.-5

Aim:-

Write a program for behavior model of BCD to Seven Segment Decoder.

SPECIFICATION OF APPARATUS USED:-

Mentor Graphics FPGA Advantage Software Modelsim Simulation Tool.

Program:-


```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_arith.all;
```

```
Entity BCD_2 is
Port (b: in bit_Vector (3 down to 0); z: out bit_vector (6 down to 0));
End BCD_2;
```

```
Architecture BCD_2_beh of BCD_2 is
```

```
Begin
Process (b)
Begin
Case B is
When "0000"=>
S<="1111110";
When "0001"=>
S<="0110000";
When "0010"=>
S <="1101101";
When "0011"=>
S<="1111001";
When "0110"=>
S<="1011111";
When"0111"=>
S<="1110000";
When"1000"=>
S<="1111111";
When"1001"=>
S<="1110011";
When other =>
S<="0000000";
End case;
End process;
End BCD_Beh;
```


EXPERIMENTAL SET UP:-

 

BCD Input's A B C D	Output's						
	a	b	c	d	e	f	g
0 0 0 0	1	1	1	1	1	1	0
0 0 0 1	0	1	1	0	0	0	0
0 0 1 0	1	1	0	1	1	0	1
0 0 1 1	1	1	1	1	0	0	1
0 1 0 0	0	1	1	0	0	1	1
0 1 0 1	1	0	1	1	0	1	1
0 1 1 0	1	0	1	1	1	1	0
0 1 1 1	1	1	1	0	0	0	0
1 0 0 0	1	1	1	1	1	1	1
1 0 0 1	1	1	1	1	0	1	1

Truth table of BCD-to-Seven Segment Decoder

 Wave Form of BCD-to-Seven Segment Decoder:-



Precautions:-

Make sure that there is no syntax and semantic error.

Result:-

All the VHDL codes of BCD to Seven Segment is simulated and synthesized.

EXPERIMENT NO.-6

Aim:-

Write a VHDL program for behavior model of PIPO.

SPECIFICATION OF APPARATUS USED:-

Mentor Graphics FPGA Advantage Software Modelsim Simulation Tool.


Program:-

```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_arith.all;
```


```
Entity PIPO_2 is
Port (Pr, Cr, Clk: in bit; D: is bit_vector (2 down to 0); Q: out bit_vector (2 down to 0));
End PIPO_2;
```

```
Architecture PIPO_2_beh of PIPO_2 is
Begin
Process (Pr, Cr, Clk, D)
Begin
If (Pr='0' and Cr='1') then
Q<='111';
Elsif (Pr='1' and Cr='0') then
Q<='000';
Elsif (Pr='0' and Cr='1') then
Q<='0';
Elsif (Pr='1' and Cr='1') then
Q<='111';
Elsif (Pr='1' and Cr='1'and Clk='0' and Clk's event) then
Q<='D;
End if;
End process;
End PIPO_2_beh;
```

 Block diagram of 4-bit Parallel in Parallel out Register



 Waveform of 4-bit Parallel in Parallel Out Register:-



Precautions:-

Make sure that there is no syntax and semantic error.

Result:-

All the VHDL codes of PIPO is simulated and synthesized.

EXPERIMENT NO.-7

Aim:-

Write VHDL programs for the following Circuit, check the wave forms and hardware generated.

- A. Half Adder.
- B. Full Adder.

SPECIFICATION OF APPARATUS USED:-

Mentor Graphics FPGA Advantage Software Modelsim Simulation Tool.

Program: -

A). Behavior Model of Half Adder:-

```
Library IEEE;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_arith.all;
```

```
Entity HA_2 is
Port (a, b: in bit; s, c: out bit);
End HA_2;
Architecture HA_2_beh of HA_2 is
Begin
Process (a, b)
Begin
If (a='0' and b='0') then
S<='0';
C<='0';
Elsif (a='0' and b='1') then
S<='1';
C<='0';
Elsif (a='1' and b='0') then
S<='1';
C<='0';
Elsif (a='1' and b='1') then
S<='0';
C<='1';
End if;
End process;
End HA_2_beh;
```


B) Behavior Model of FULL Adder:-

```

Library IEEE;
  Use ieee.std_logic_1164.all;
  Use ieee.std_logic_arith.all;
Entity FA_2 is
  Port (a, b, cin: in bit; s, c: out bit);
End FA_2;
Architecture FA_2_beh of FA_2 is
Begin
  Process (a, b, cin)
  Begin
    S<=a XOR B XOR Cin;
    C<=(a and b) OR (a and cin) OR (b and cin);
  End process;
End FA_2_beh;

```


EXPERIMENTAL SET UP:-

 

Input's			Output's	
A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth table of Full Adder

Wave Form:-

 

Precautions:-

Make sure that there is no syntax and semantic error.

Result:-

- A) All the VHDL codes of Half Adder is simulated and synthesized.
- B) All the VHDL codes of Full Adder is simulated and synthesized.

EXPERIMENT NO.-8

Aim:-

Write VHDL programs for ALU.

SPECIFICATION OF APPARATIUS USED:-

Mentor Graphics FPGA Advantage Software Modelsim Simulation Tool.

Program: -


Behavior Model of ALU.

```
Library IEEE;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_arith.all;
```

```
Entity ALU_2 is
Port (p, q: in bit_vector (3 down to 0); s: in bit_vector (2 down to 0); f: in bit_vector (3 down to 0));
End ALU_2;
Architecture ALU_2_beh of ALU_2 is
Function of "+"
Function add (a, b: bit_vector (2 down to 0)
Return bit_vector is
Variable cout: bit;
Variable cin: bit;
Variable sum: bit_vector (2 down to 0);
Begin
For i: in 0 to 2 loop
Sum (i): a (i) XOR b (i) XOR Cin;
Cout: = (a (i) and b (i)) OR (b (i) and Cin) OR (Cin And a (i));
Cin: = Cout
End loop;
Return sum;
End "+"
--function of subtraction of 2 bit array
Function "-"(a, b: bit_vector (3 down to 0
Return bit_vector is
Variable cout: bit;
Variable Cin: bit='0';
Variable diff (i): bit_vector (3 down to 0);
Begin
For I in 0 to 3 loop
Cout: = ((not a (i) and b (i)) or ((b (i) and cin) or ((not a (i) and cin)) ;
Diff (i):= a (i) xor b (i) xor cin;
```

```
Cin: = cout;  
End loop;  
Return diff (i);  
End “-“;  
  
Begin  
Process (p, q, and s)  
Begin  
Case s is  
When “000”=>  
F<= “0000”;  
When “001” =>  
F =q-p;  
When “010”=>  
F =p-q;  
When “001”=>  
F =p+q;  
When “100”=>  
F =p and q;  
When “101”=>  
F<= p xor q;  
When “110”=>  
F<=p or q:  
When “111” =>  
F<= “1111”;  
End case;  
End process;  
End ALU_Beh;
```


EXPERIMENTAL SET UP:-

 

Select Input S2 S1 S0	Operation	Output F
0 0 0	CLEAR	0 0 0 0
0 0 1	Q - P	Q - P
0 1 0	P - Q	P - Q
0 1 1	ADD	P + Q
1 0 0	XOR	P XOR Q
1 0 1	OR	P OR Q
1 1 0	AND	P AND Q
1 1 1	PRESET	1 1 1 1

Function Table of ALU(74381)

Waveform of ALU:-

 

EXPERIMENT NO.-9

Aim:-

Write a VHDL program for behavior model of D Flip-Flop.

SPECIFICATION OF APPARATUS USED:-

Mentor Graphics FPGA Advantage Software Modelsim Simulation Tool.

Program:-


```
Library IEEE;
  Use IEEE.std_logic_1164.all;
  Use IEEE.std_logic_arith.all;

Entity DIFF_2 is
  Port (Pr, Cr, Clk: in bit; D: is bit_vector (2 down to 0); Q: out bit_vector (2 down to 0));
End DIFF_2;

Architecture DIFF_2_beh of DIFF_2 is
Begin
  Process (Pr, Cr, Clk, D)
    Begin
      If (Pr='0' and Cr='1') then
        Q<='1';
      Elsif (Pr='1' and Cr='0') then
        Q<='0';
      Elsif (Pr='1' and Cr='1'and Clk='0' and Clk's event) then
        Q<=D;

      End if;
    End process;
  End DIFF_2_beh;
```


EXPERIMENTAL SET UP:-

 

PR	CR	D(i/p)	Output Q(t + 1)
0	0	X	1
0	1	X	1
1	0	X	0
1	1	0	0
1	1	1	1

Truth table of D flip-flop

Waveforms of D flip flop:-

 

Precautions:-

Make sure that there is no syntax and semantic error.

Result:-

All the VHDL codes of D-Flip-Flop is simulated & synthesized.

EXPERIMENT NO.-10

Aim:-

Write a VHDL program for behavior model of 3- Bit UP Counter.

SPECIFICATION OF APPARATUS USED:-

Mentor Graphics FPGA Advantage Software Modelsim Simulation Tool.

Program:-

```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_arith.all;
```

```
Entity COUNTER_2 is
Port (Pr, Cr, Clk, t: in bit; Q: out bit_vector (0 to 2));
End DIFF_2;
```


```
Architecture COUNTER _2_beh of COUNTER _2 is
Function of “+”
Function add (a, b: bit_vector (0 down to 2))
Return bit_vector is
Variable cout: bit;
Variable cin: bit:= ‘0’;
Variable sum: bit_vector (0 to 2):= “000”;
Begin
For i: in 0 to 2 loop
Cout:= (a (i) and b (i)) OR (b (i) and Cin) OR (Cin And a (i));
Sum (i): a (i) XOR b (i) XOR Cin;
Cin:= Cout
End loop;
Return sum;
End “+”;
Begin
Process (Clk, Pr, Cr)
Begin
If (Pr=’0’ and Cr=’1’) then
Q<= ‘111’;
Elsif (Pr=’1’ and Cr=’0’) then
Q<= ‘000’;
Elsif (Pr=’1’ and Cr=’1’and Clk=’0’ and Clk’s event) then
Q<=Q+ “000”;
```

```


End if;
End process;
End COUNTER _2_beh

```

EXPERIMENTAL SET UP:-

 

Waveform of 3-bit Up Counter:-

 

Precautions:-

Make sure that there is no syntax and semantic error.

Result: - All the VHDL codes of D-Flip-Flop is simulated & synthesized.